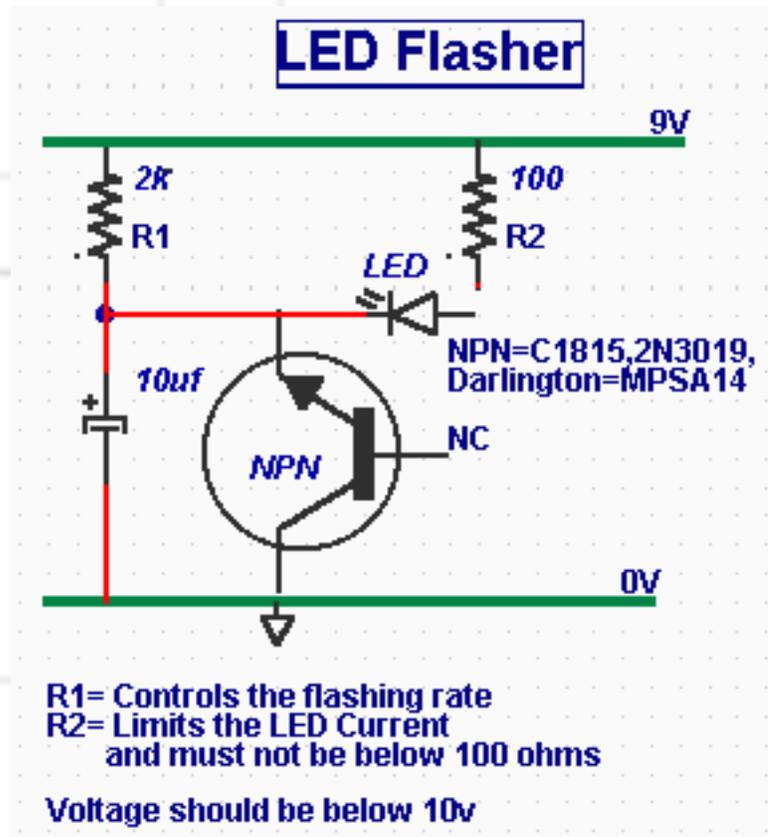





Handy Dandy #6 Little Circuits

A very simple substitute for a UJT. Not all transistors will work at 9v but dig into your junk box and give it a try. Transistors like C1815, 2N3019 and many similar will work, can also be used to monitor your battery supply, Do not use with and audio circuit on the same supply line as it will insert noise into you audio line.



The addition of a small Negative converter is nice to have when needed for those AC signals that need a few op-amps with dual supply.

POS to NEG Converter

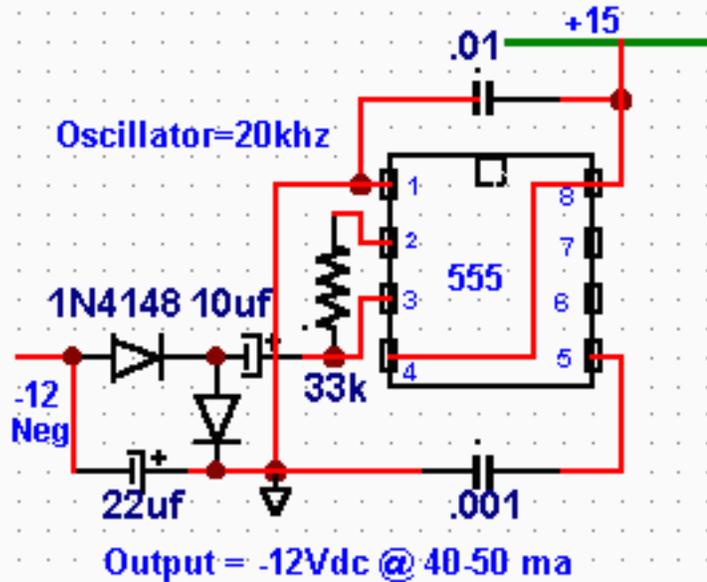

[Home](#)

Questions? Email me at roma60@home.com

© Laurier Gendron, Burnaby, B.C., Canada. 1998