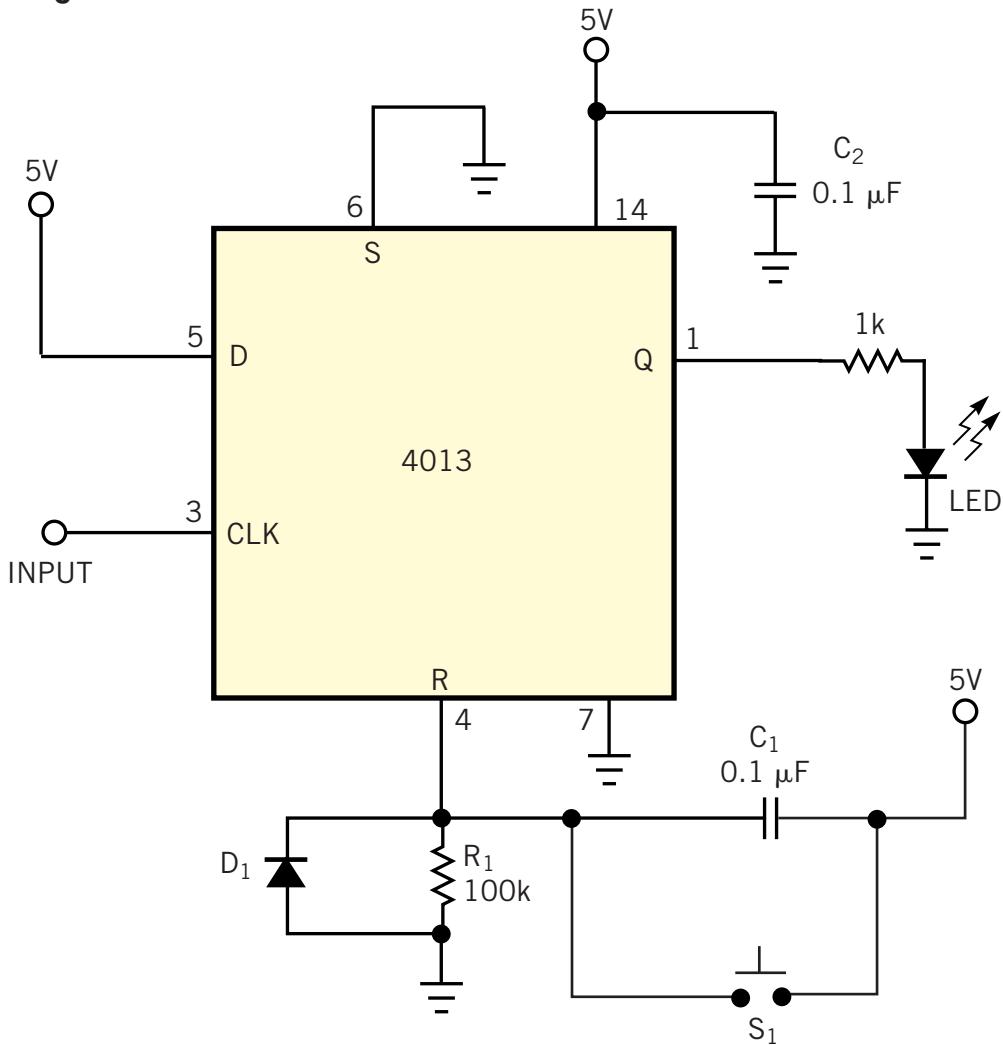


Figure 1



NOTES:

LED=HIGH-EFFICIENCY RED LED.

D_1 =IN4001 OR ANY OTHER SMALL-SIGNAL DIODE.

S_1 =OPTIONAL MOMENTARY PUSHBUTTON SWITCH.

TIE UNUSED INPUTS TO GROUND.

A 4013 CMOS flip-flop and a handful of passive components monitor the activity of an embedded system's watchdog reset.