

## **Application Note OA-18**

# **Simulation SPICE Models** for Comlinear's Op Amps

May 2000

## This application note is updated as new products are released. Please check with National Semiconductor for the latest version.

National Semiconductor Corporation is a manufacturer and supplier of high-performance analog signal processing components. National's broad signal conditioning product line includes high-speed hybrid and monolithic operational amplifiers, buffers, video amplifiers, multiplexers, automatic gain control integrated circuits, track/hold amplifiers, and analog-to-digital converters. National continues as a leader in developing products offering exceptional performance, speed, quality, reliability and service.

#### INTRODUCTION

This is a collection of PSpice compatible models for National Semiconductor Corporation amplifiers. For additional information about SPICE Models supporting existing or new products, customers can visit National's web site at http://www.national.com. These SPICE Models are created for use on an IBM compatible computer using analysis programs that accept Spice formats. National assumes no responsibility for designs created from these SPICE Models. These SPICE Model files model typical performance at room temperature. AC response is dominated by board layout and package parasitics at frequencies above 500MHz. Before designs are released to production, National suggests that topologies be verified by prototyping the circuit. The part-to-part and over-temperature performance variations of National amplifiers are specified in current data sheets found on National's web site. The changes from the last SPICE Model version are listed in this table:

## TABLE I. UPDATES TO SPICE MODELS

CLC405.CIR CLC406.CIR CLC407.CIR	A new SPICE Model. A revised SPICE Model. A new SPICE Model.
CLC412.CIR	A new SPICE Model.
CLC430.CIR	A revised SPICE Model that improves
	disabled output response.
CLC440.CIR	A new SPICE Model.
CLC449.CIR	A new SPICE Model.
CLC450.MOD	A new SPICE Model.

#### TABLE II. SPICE MODEL SUBCIRCUIT FILES

File Name	Description
CLC109.CIR	A Low-Power, Wideband, Closed-Loop Buffer.
CLC111.CIR	A Very Wideband, Ultra-High Slew Rate,
	Closed-Loop Buffer.
CLC400.CIR	A Wideband, Low-Gain Monolithic Current
	Feedback Op Amp with Fast Settling,
	(0.05% in 12ns), Low Power and an Input
	Offset Adjustment Pin.
CLC401.CIR	A Wideband, High-Gain Monolithic Current
	Feedback Op Amp with Fast Settling
	(0.01% in 10ns) and Low Power.
CLC402.CIR	A Low-Gain Monolithic Current Feedback
	Op Amp with Fast 14-bit Settling (0.0025%
	in 25ns) and Low Power.
CLC404.CIR	A Wideband Monolithic Current Feedback
a. a a	Op Amp with High Slew Rate.
CLC405.CIR	A Low-Cost, Low Power, 110MHz Op Amp
01 0 100 015	with Disable.
CLC406.CIR	•
01 0 407 010	Current Feedback Op Amp.
CLC407.CIR	A Low-Cost, Low Power, Programmable
01 0 400 010	Gain Buffer with Disable.
CLC409.CIR	A Very Wideband, Low Distortion Monolithic
01 0440 010	Current Feedback Op Amp.
CLC410.CIR	
	Amp with disable, Fast Settling (0.05% in
CLC412.CIR	12ns) and an Input Offset Adjust Pin.
CLC412.CIR	A Dual Wideband Video Op Amp. A Quad, Low-Power Monolithic Current-
CLC414.CIR	Feedback Op Amp.
CLC415.CIR	A Quad Wideband Monolithic Current
CLC4 15.CIR	
CLC420.CIR	Feedback Op Amp.  A High Speed Unity Gain Stable Manelithic
CLC420.CIR	A High-Speed, Unity Gain Stable Monolithic Voltage Feedback Op Amp.
CLC425.CIR	An Ultra Low-Noise, Wideband Monolithic
CLC423.CIR	Voltage Feedback Op Amp with Current
	Supply Adjust.
	Supply Aujust.

CLC426.CIR An Ultra Low-Noise, Wideband Monolithic

CLC428.CIR An Ultra Low-Noise, Wideband, Dual

CLC430.CIR A Wideband Monolithic Current Feedback

supply capability.

Voltage Feedback Op Amp with Current Supply Adjust and External Compensation.

Monolithic Voltage Feedback Op Amp.

Op Amp with disable and ±5V to ±15V

TABLE II. SPICE MODEL SUBCIRCUIT FILES		
File Name	Description	
CLC431.CIR	A Dual, Wideband Monolithic Current Feedback Op Amp with high slew rate.	
CLC432.CIR	A Dual, Wideband Monolithic Current Feedback Op Amp with disable and ±5V to ±15V supply capability.	
CLC440.CIR	A High-Speed, Low-Power Voltage Feedback Op Amp.	
CLC449.CIR	• •	
CLC450.MOD	A Single Supply, Low Power, High Output, Current Feedback Amplifier	
CLC501.CIR	A High-Speed Output Clamping Monolithic Current Feedback Op Amp for high gains.	
CLC502.CIR		
CLC505.CIR		
CLC520.CIR	·	
CLC522.CIR	A Monolithic Wideband Variable Gain Amplifier.	

- tage
- Gain
- CLC532.CIR A High-Speed, 2:1 Analog Multiplexer with fast 12-bit settling (0.01% in 17ns), low noise, low distortion and adjustable noise bandwidth.
- CLC5644.CIR A Quad, Low-Power Monolithic Current-Feedback Op Amp.
- CLC5655.CIR A Quad Wideband Monolithic Current Feedback Op Amp.
- CLC5665CIR A Wideband Monolithic Current Feedback Op Amp with disable and ±5V to ±15V supply capability.
- CLC5801CIR An Ultra Low-Noise, Wideband Monolithic Voltage Feedback Op Amp with Current Supply Adjust.
- CLC5802.CIR An Ultra Low-Noise, Wideband, Dual Monolithic Voltage Feedback Op Amp.

#### START UP INSTRUCTIONS

Download all SPICE Model files of interest to a library on the hard disk. If the library directory is not in the SPICE program's path, the user should set that path in the autoexec.bat for easier excess. The .INC statement in PSpice should be used in the simulation file to include the SPICE Models subcircuit.

Example: ".INC CLC400.CIR"

#### **AMPLIFIER SPICE MODELS**

These SPICE Model files are written in ASCII file format for IBM-compatible PC's. They are compatible with PSpice and other Spice 2G simulators. For additional detailed information about using PSpice please contact MicroSim (See Reference below). National amplifier SPICE Models are written in a subcircuit format for easy incorporation into larger circuits. A listing of any amplifier subcircuit may be obtained by printing its CLC\*.CIR file to a local printer. The subcircuit node assignments match the device pin-outs as shown in the individual device data sheets. An example is an 8 pin op amp.

- Connections: NON-INVERTING INPUT PIN
- | INVERTING INPUT PIN
- | | OUTPUT
- | | | +Vcc
- | | | | -Vcc
- | | | | |
- .SUBCKT (NAME) 32674

Some schematic capture software packages require a different pin connection order than what National uses. Changing the pin order in the .SUBCKT statement will not affect the SPICE Model performance.

#### PERFORMANCE RESULTS

When substitutions of current feedback op amps are made for voltage feedback op amps, results may not be acceptable. Refer to National 's application note OA-13 for a tutorial on current feedback op amp design.

#### PARAMETERS MODELED

The following typical performance parameters are modeled by the SPICE Models.

#### **DC Effects**

- VIO, IBI, IBN
- Supply current vs. supply voltages
- Common mode input/output voltage range
- Load current from supplies
- CMRR

#### AC Effects < 500MHz

- Frequency response vs. gain & load
- Open loop gain & phase
- Noise
- Small signal input/output impedance

#### **Time Domain**

- Rise/fall times
- Slew rates

## Special Features (where applicable)

- Output clamping
- Supply current adjustment
- Offset voltage adjust
- Disable/enable times
- External compensation

#### PARAMETERS NOT MODELED


- Differential gain and phase
- PSRR
- Harmonic distortion
- Fine scale settling performance
- Thermal tail
- Overdrive recovery time (Except for the CLC501and the CLC502)
- Variation in performance vs. temperature
- Part-to-part performance variation


#### REFERENCES


- 1) National 's 1993/1994 Databook and 1995 Databook Supplement of standard products.
- 2) MicroSim Corporation, 20 Fairbanks, Irvine, CA 92718 USA, (714) 770-3022, (800) 245-3022.

## **NOTICE**


The information provided within these files and documents is believed to be reliable and correct. National assumes no responsibility for alterations, omissions or inaccuracies. National assumes no responsibility for the use of this information, and all use of such information shall be entirely at the user's own risk. National does not grant licenses or patent rights to any of the circuits described within this document.

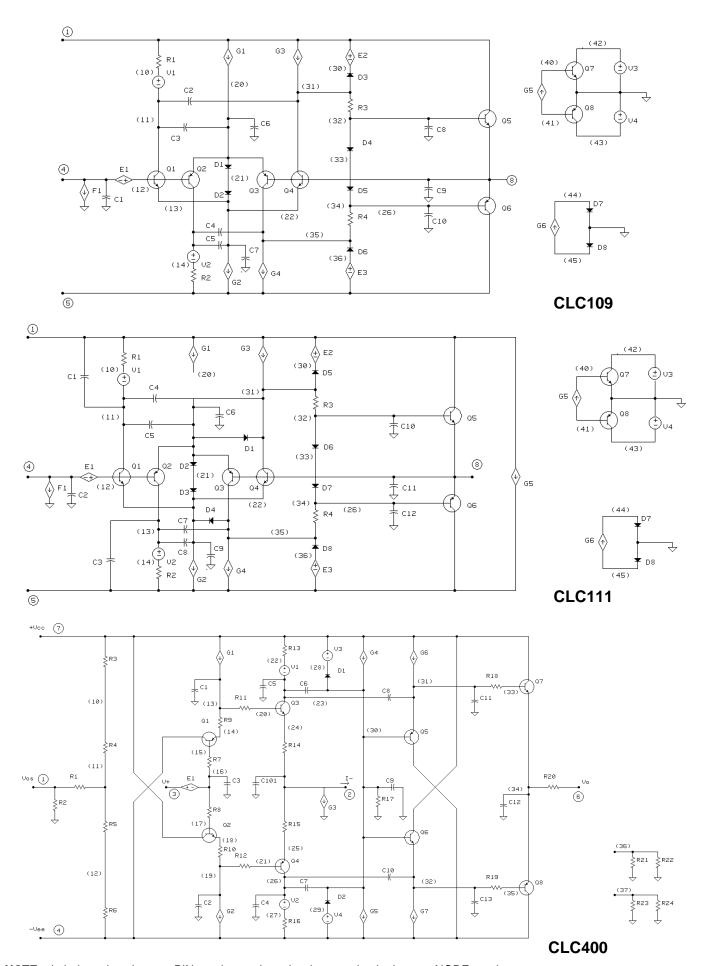


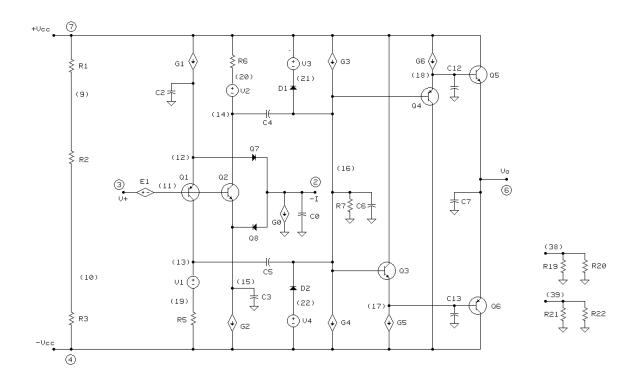


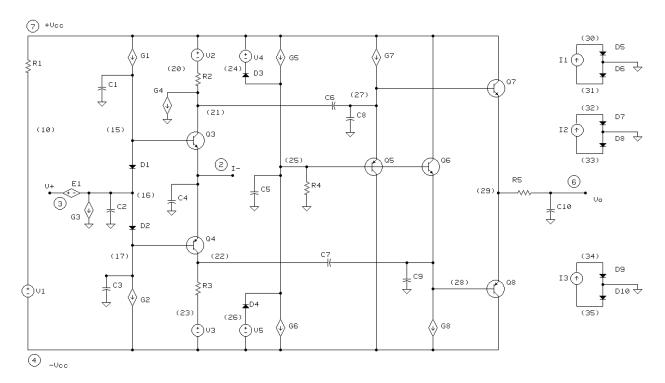



**CLC402** 

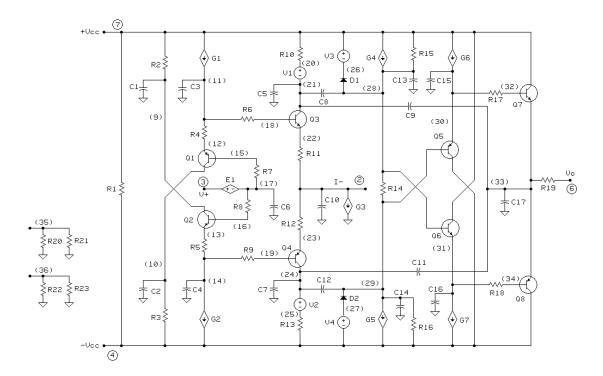


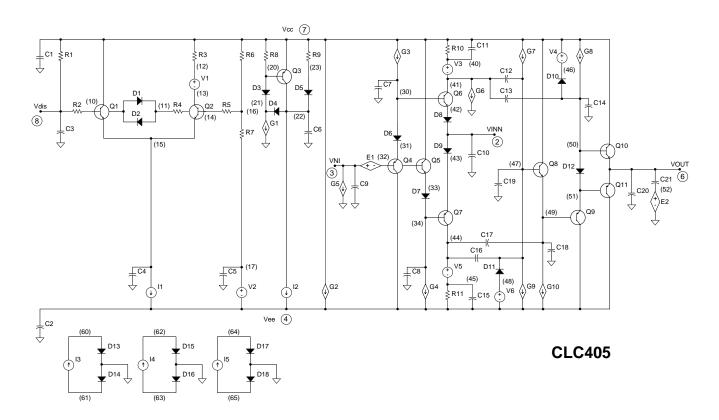

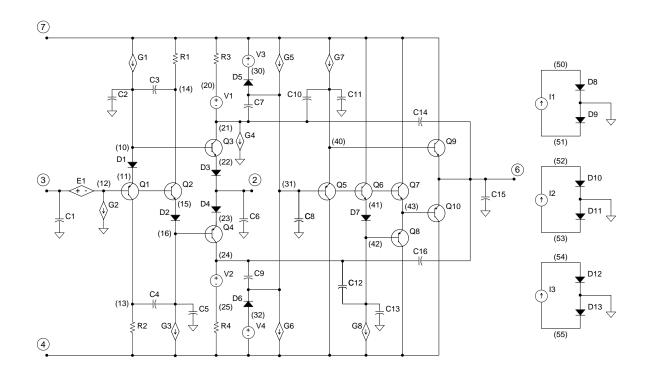

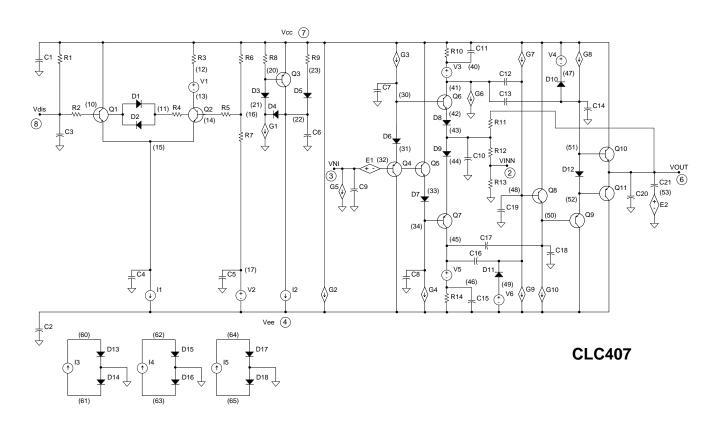


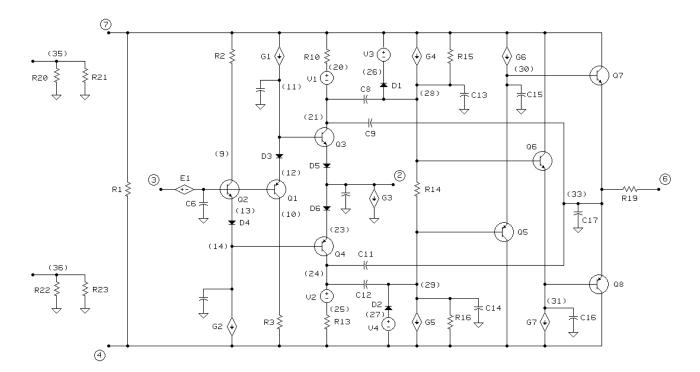


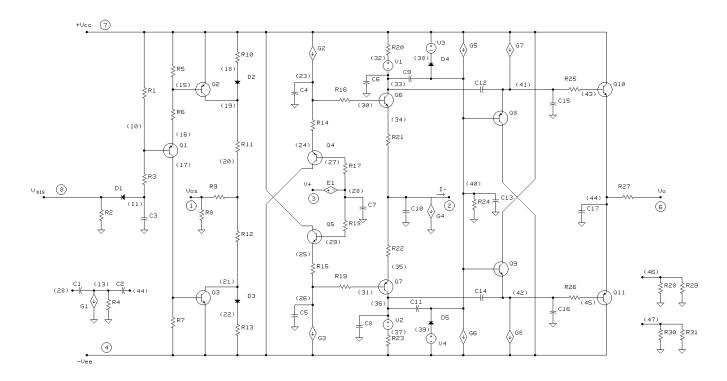


8


**CLC410** 

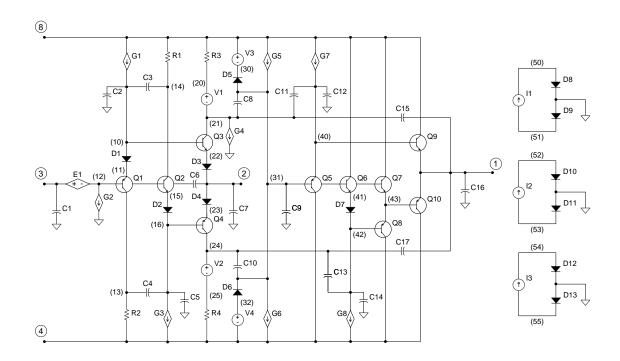

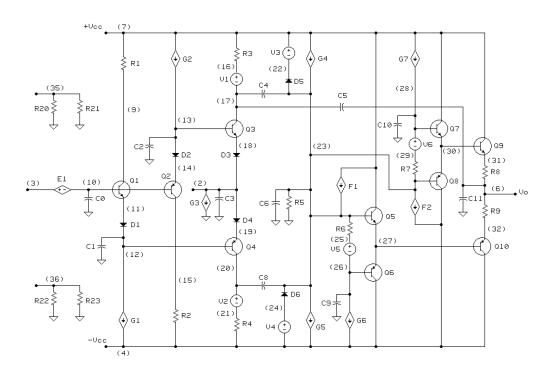



## **CLC414**

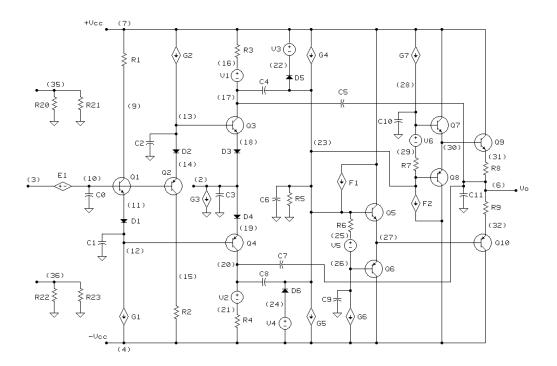


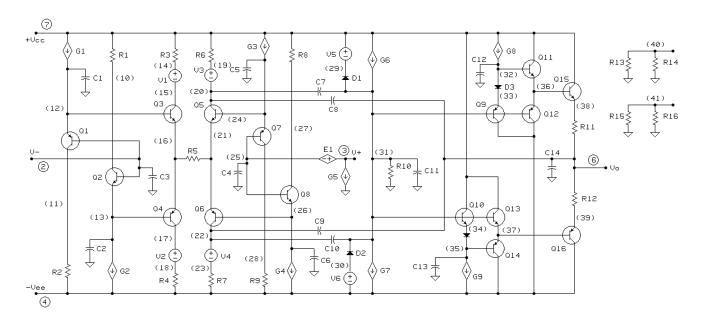


**CLC420** 

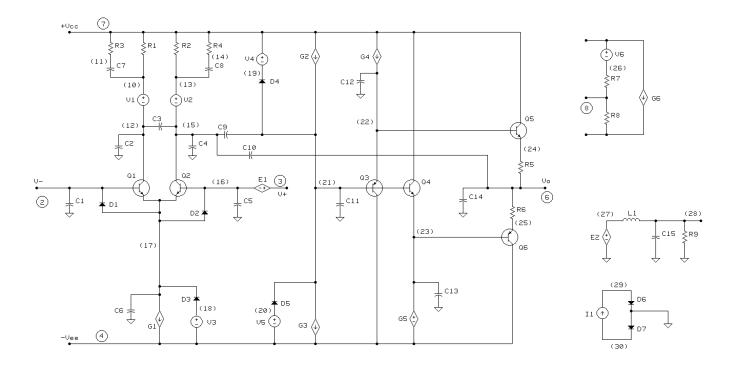

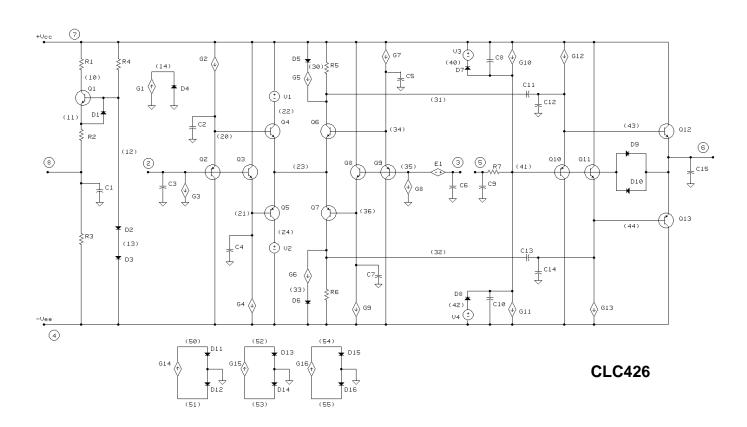


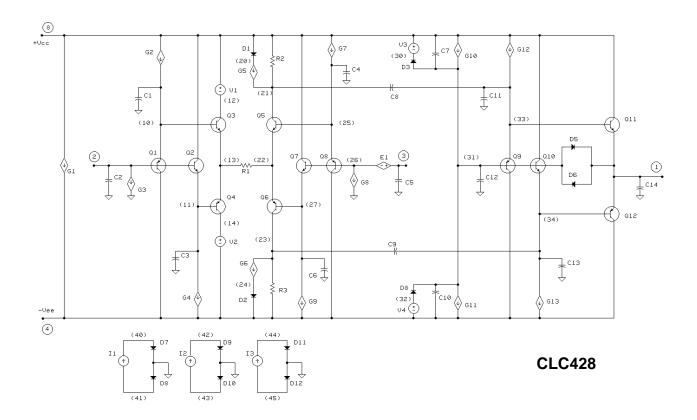


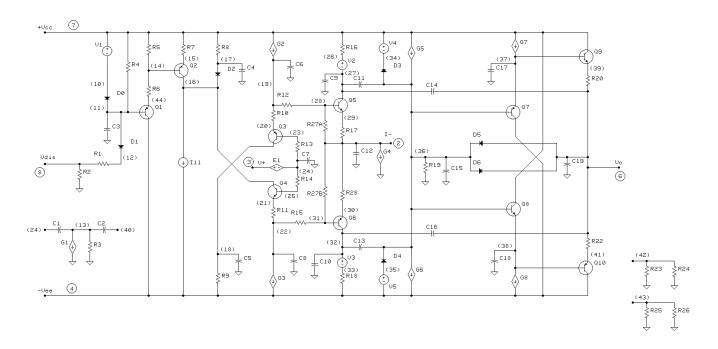



12

**CLC430** 

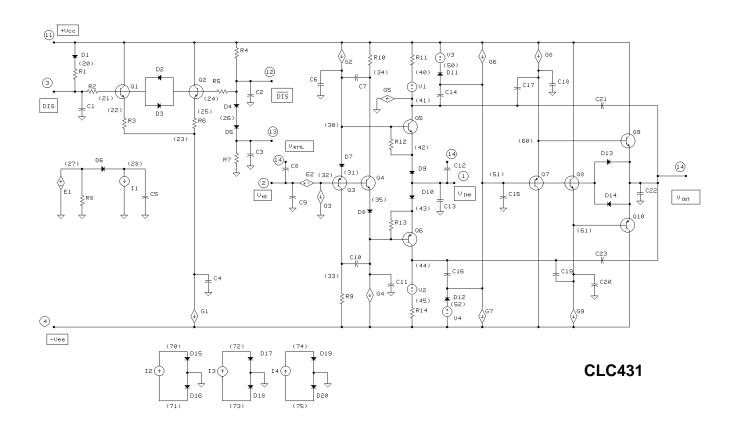


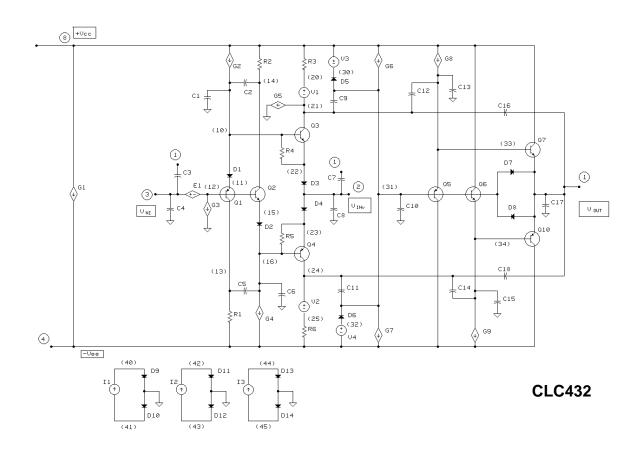


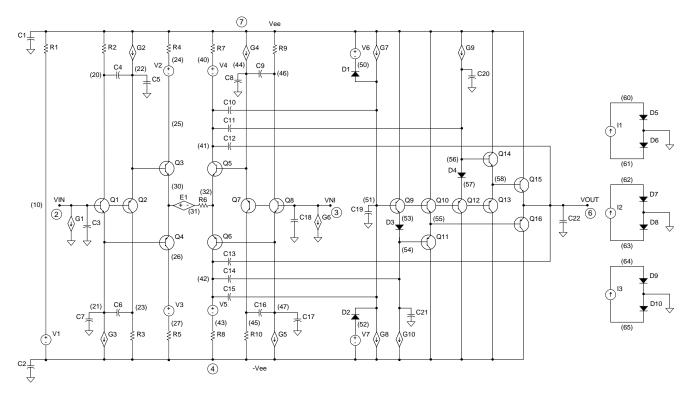

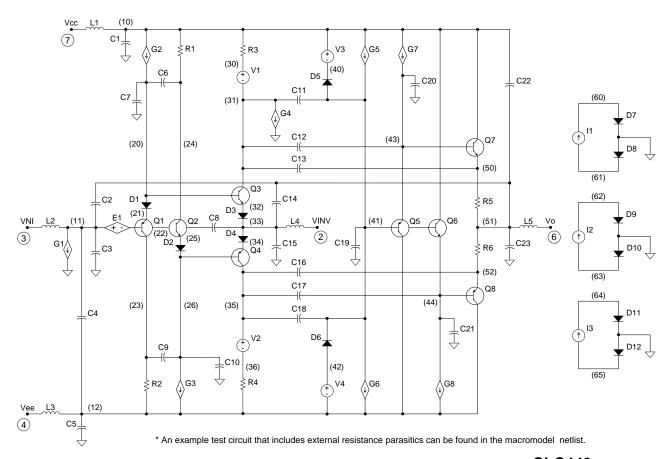



**CLC449** 

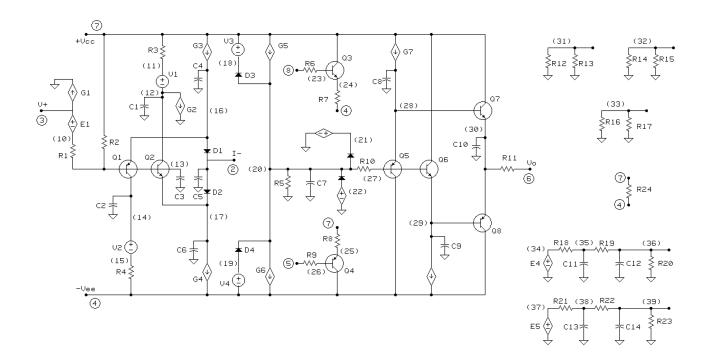

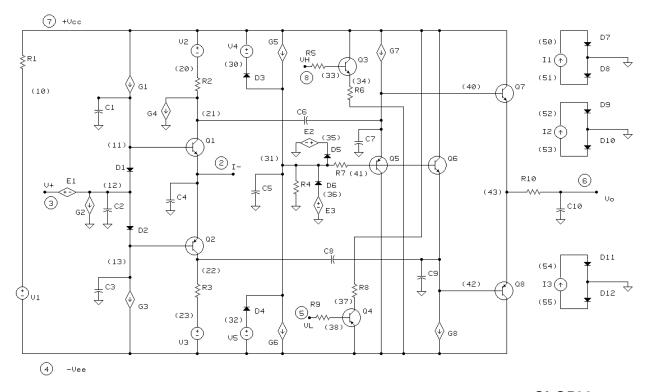



**CLC502** 

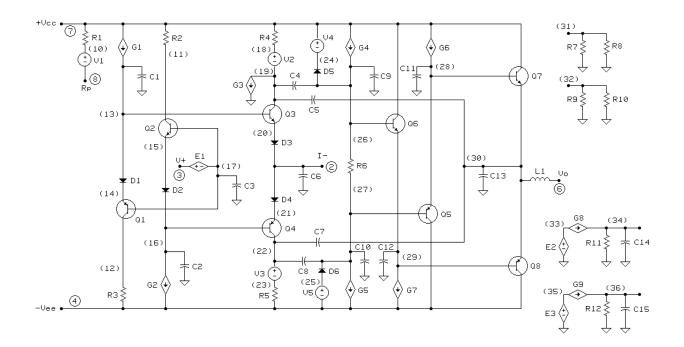

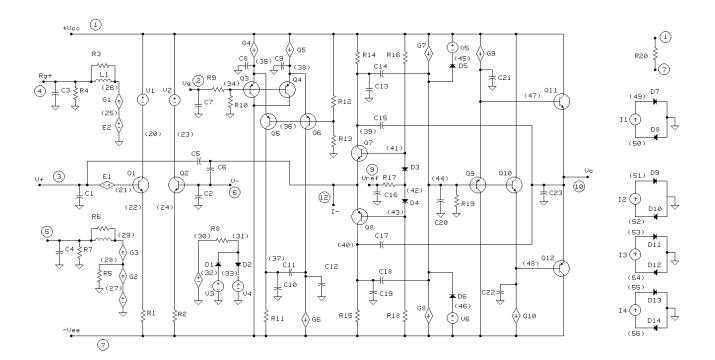



**CLC520** 

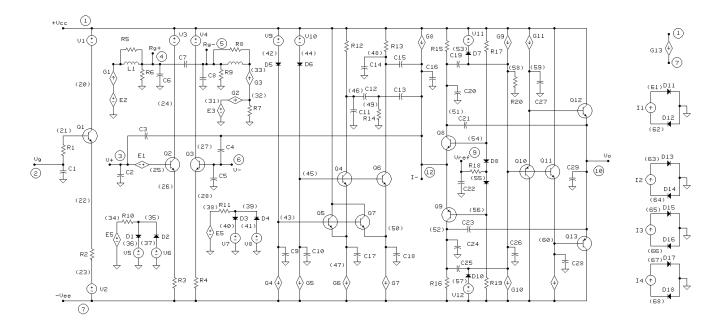

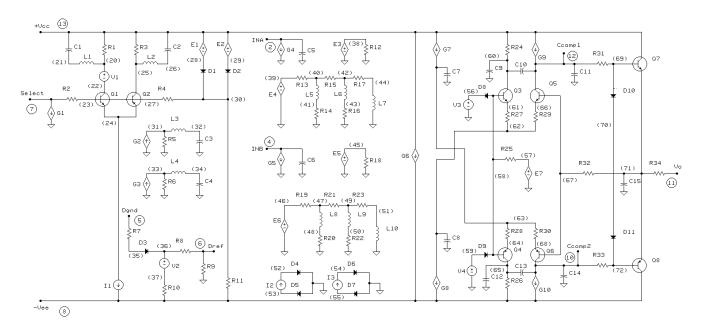

**CLC532** 

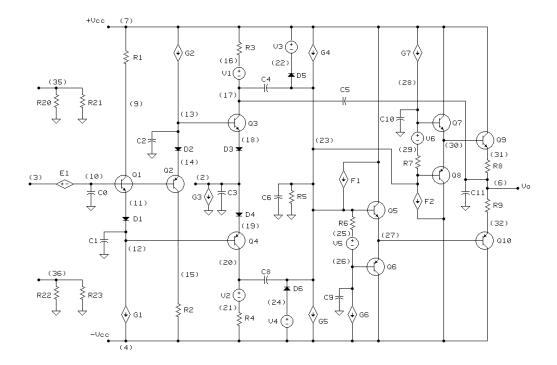


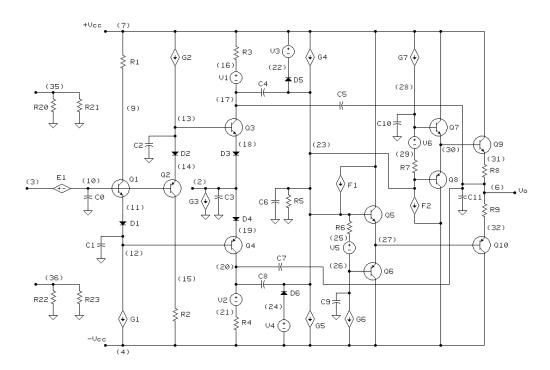


**CLC5654** 


**NOTE:** circled number denotes PIN number and number in parenthesis denotes NODE number.

http://www.national.com 18

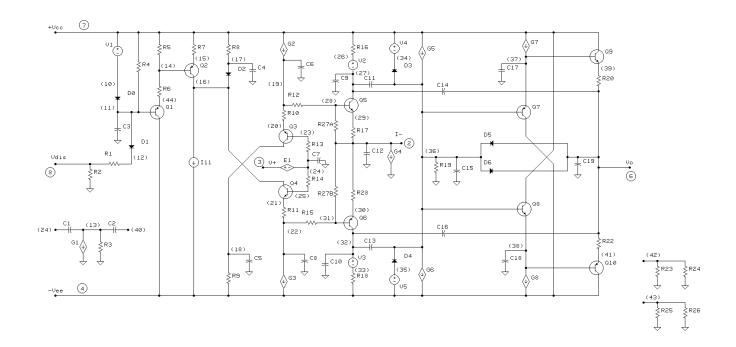

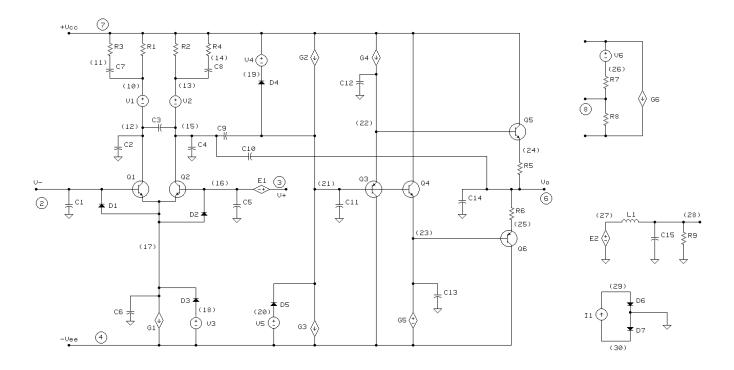

**CLC5801** 

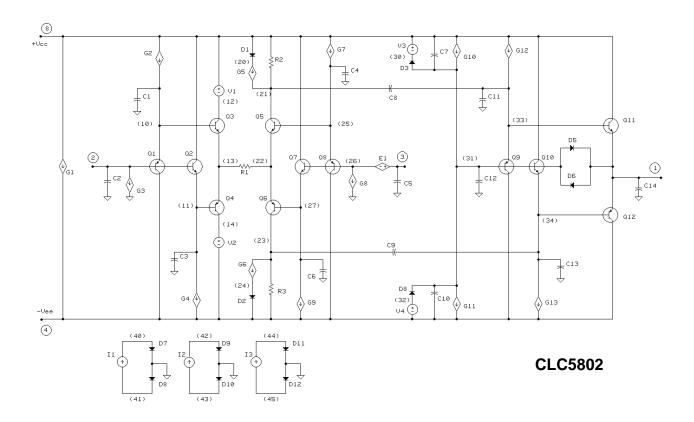

NOTE: circled number denotes PIN number and number in parenthesis denotes NODE number.

## LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- 1. Life support devices or systems are devices or systems which, a) are intended for surgical implant into the body, or b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



#### National Semiconductor Corporation Americas

Tel: 1(800) 272-9959 Fax: 1(800) 737-7018 Email: support@nsc.com

## National Semiconductor Europe

Fax: +49 (0) 1 80-530 85 86 E-mail: europe.support.nsc.com Deutsch Tel: +49 (0) 1 80-530 85 85 English Tel: +49 (0) 1 80-532 78 32 Francais Tel: +49 (0) 1 80-532 93 58 Italiano Tel: +49 (0) 1 80-534 16 80

## National Semiconductor Asia Pacific Customer Response Group

Fax: 65-2504466 Email: sea.support@nsc.com

Tel: 65-25-2544466

#### National Semiconductor Japan Ltd.

Tel: 81-3-5639-7560 Fax: 81-3-5639-7507